
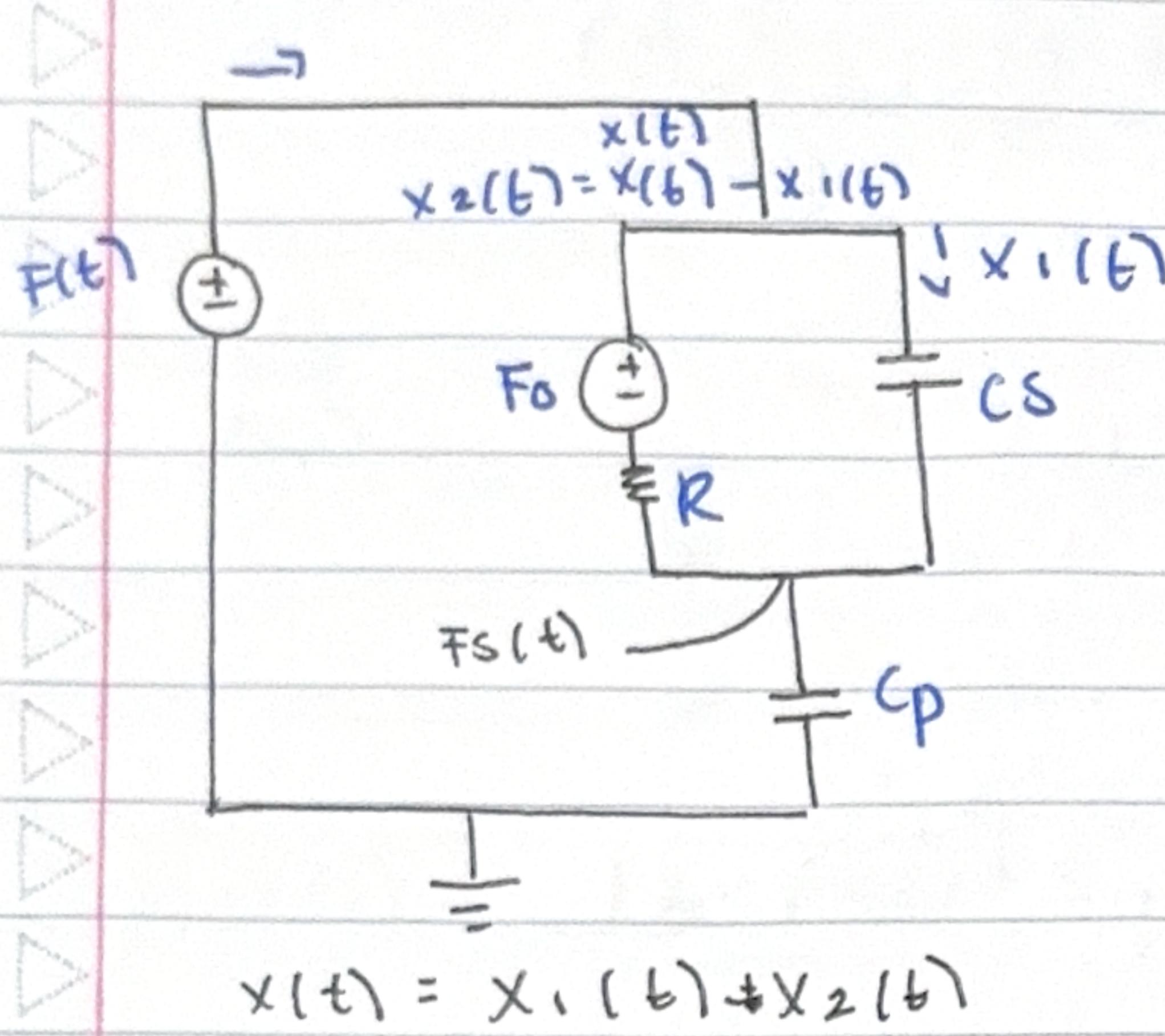


Cto. eléctrico

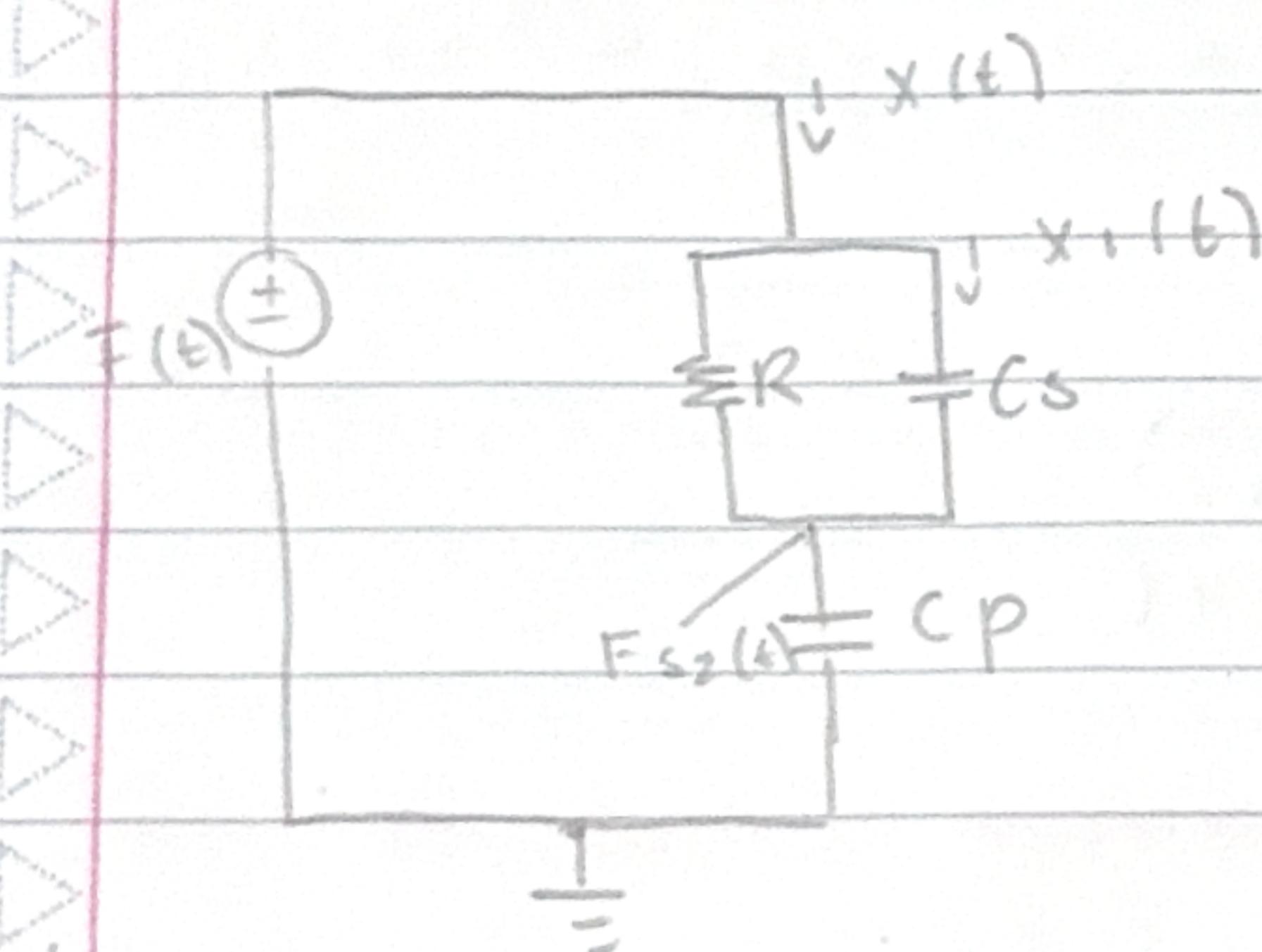

Función de transferencia

Análisis apagando F_0 

por
nodos
integrales

$$x(t) = \frac{d[F_S(t)]}{dt} C_P$$

$$x_2(t) = \frac{F(t) - F_S(t)}{R}$$

$$x_1(t) = C_S \frac{d[F(t) - F_S(t)]}{dt}$$

$$C_P \frac{dF_S(t)}{dt} = C_S \frac{d[F(t) - F_S(t)]}{dt} + F(t) - F_S(t)$$

IC

Transformada de Laplace

$$C_p S F_S(s) = C_s S [F(s) - F_S(s)] + F(s) - F_S(s)$$


$$(C_p S + (sS + \frac{1}{R})) F_S(s) = ((sS + \frac{1}{R}) F(s))$$

$$\frac{F_S(s)}{F(s)} = \frac{CsS + \frac{1}{R}}{CsS + \frac{1}{R} + C_p S} = \frac{(CsR + 1)}{(CsR + CsR^2 + C_p R)S + 1}$$

$$G \frac{CsS R + 1}{R}$$

$$\frac{CsS + 1}{R} = \frac{CsS + 1}{R} \quad \text{desarrollando el numerador}$$
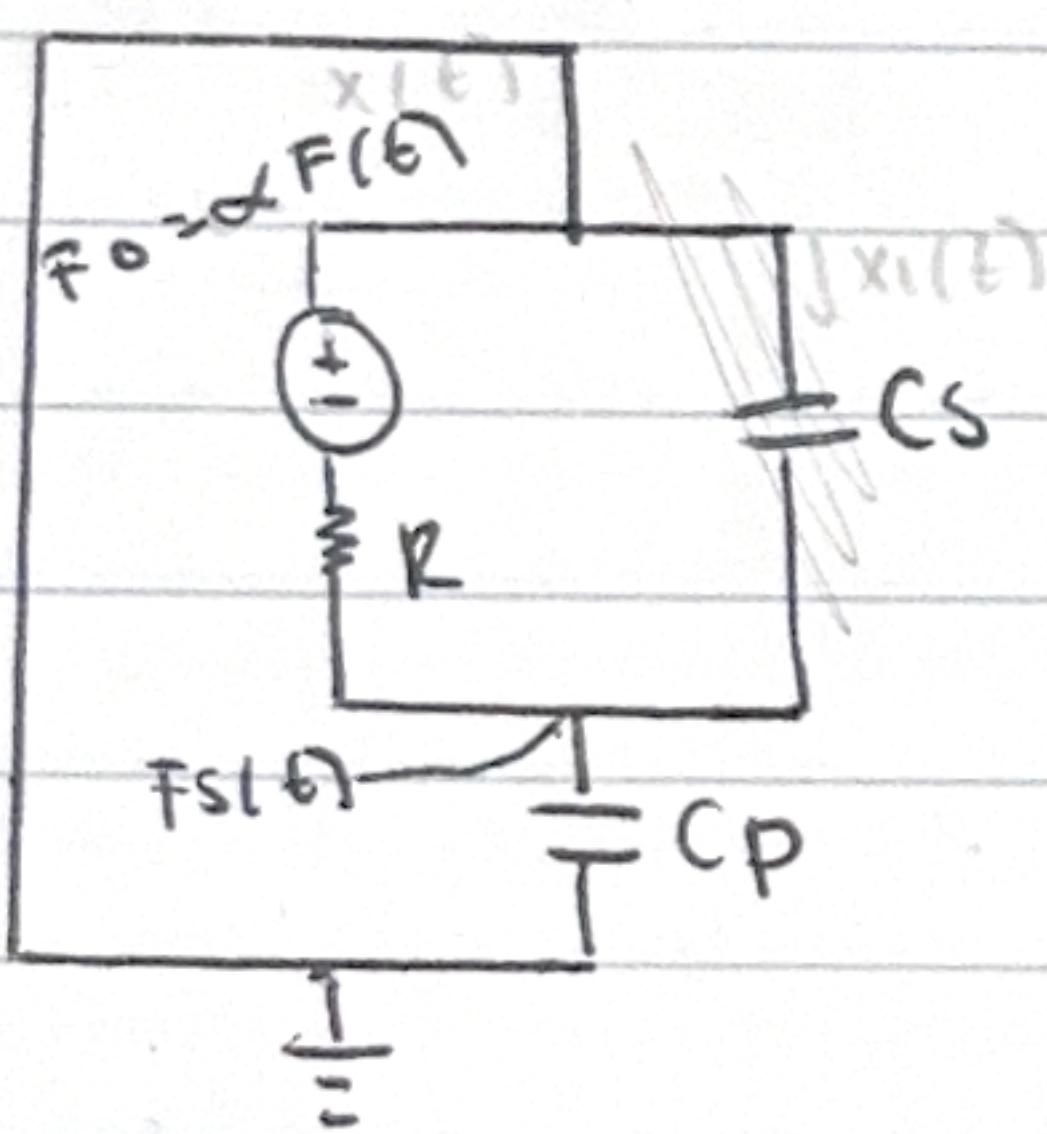
$$\frac{C_p S + C_s S R + 1}{R^2} = \frac{C_p S R + C_s S R^2 + R}{R^2}$$




$$F_{\text{out}}(s) = (CsR s + 1) F(s)$$

$$R / (Cs + C_p) s + 1$$

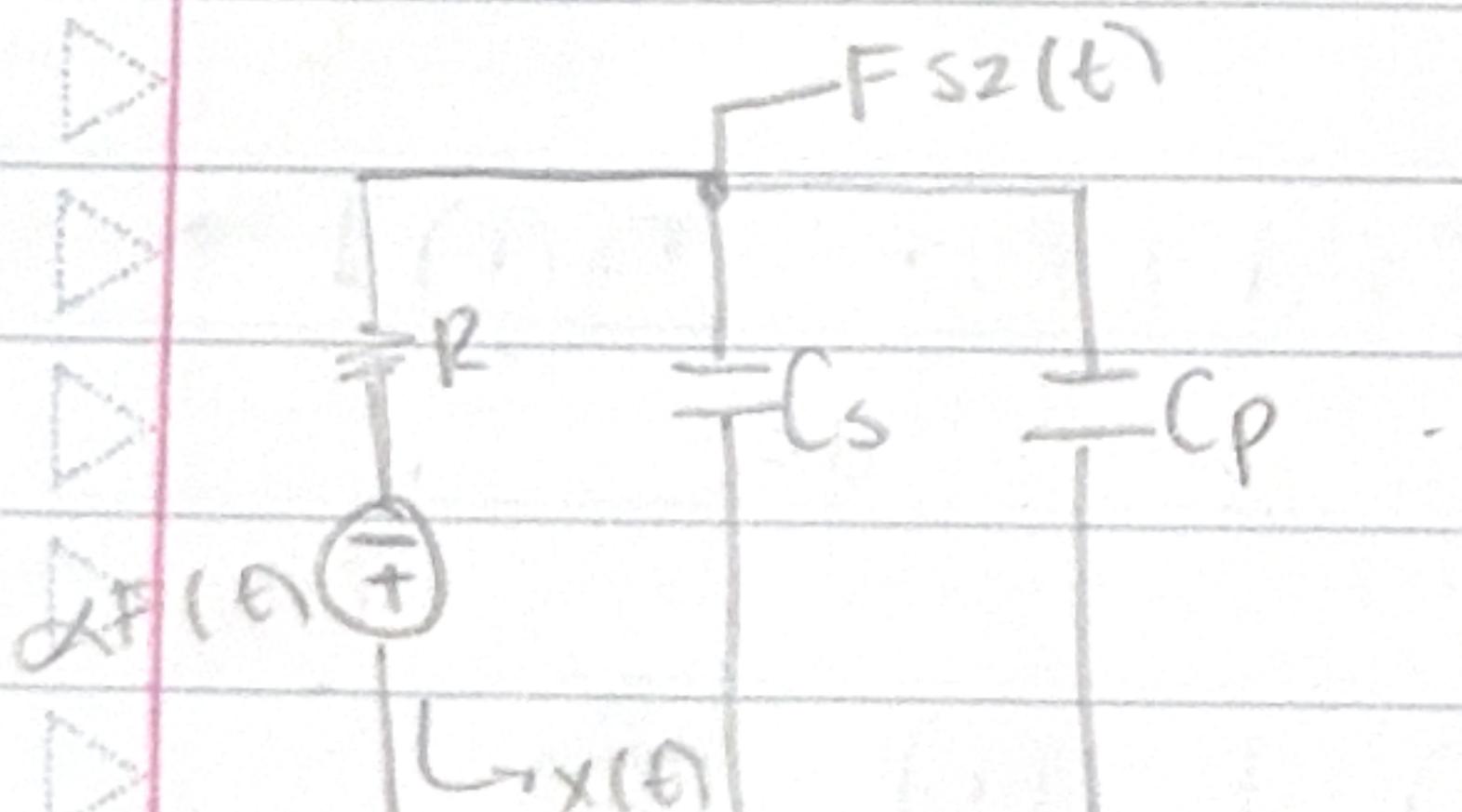F. de transferencia


$$-\alpha F(t) = R x(t) + \frac{1}{Cs + C_p} \int x(t) dt$$



$$F_S(t) = \frac{1}{Cs + C_p} \int x(t) dt$$

Transformada de Laplace
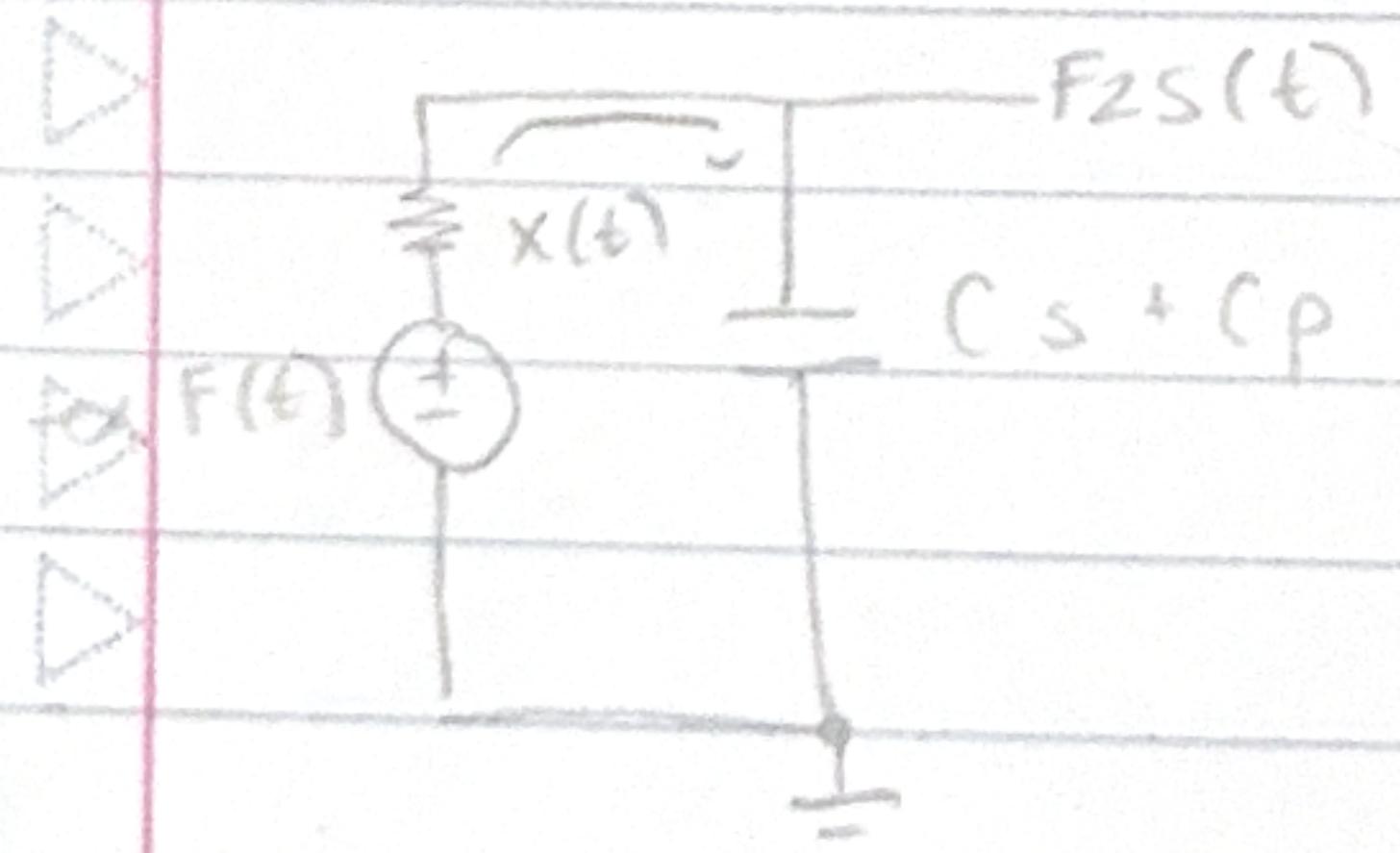
$$-\alpha F(s) = R x(s) + \frac{x(s)}{(Cs + C_p)s}$$



$$F_{\text{out}}(s) = \frac{x(s)}{(Cs + C_p)s}$$

$$F(s) = -\frac{R(cs+cp)s + 1}{\alpha(cs+cp)s} x(s)$$

$$\frac{Fs(s)}{F(s)} = \frac{\frac{x(s)}{(cs+cp)s}}{\frac{R(cs+cp)s + 1}{\alpha(cs+cp)s} x(s)} = -\frac{\alpha}{R(cs+cp)s + 1}$$

$$Fs_2(s) = -\frac{\alpha F(s)}{R(cs+cp)s + 1}$$

$$Fs(s) = F_{21}(s) + Fs_2(s)$$

$$Fs(s) = \frac{(CsRs + 1)F(s) - \alpha F(s)}{R(cp + (s)s + 1)}$$

Error est.
est. en lazo ab.

$$\frac{Fs(s)}{F(s)} = \frac{CsRs + 1 - \alpha}{R(cp + (s)s + 1)} = -\frac{\alpha}{R(cs+cp)s + 1}$$

Error en estado estacionario

$$e(s) = \lim_{s \rightarrow 0} s f(s) \left[1 - \frac{Fs(s)}{F(s)} \right] \quad e(s) = \alpha \\ e(t) = \alpha v$$

$$e(s) = \lim_{s \rightarrow 0} s \cdot \frac{1}{s} \left[1 - \frac{CsRs + 1 - \alpha}{R(cs+cp)s + 1} \right]$$

Estabilidad en lazo abierto

$$R(cp + (s)s + 1) = 0$$

$$\lambda = -\frac{1}{R(cp + (s)s)}$$